

**DESIGN A PD controller for a given rlc circuit to
IMPROVE it's SETTLING TIME.**

Team Member:

Name

ID

1. Shah Jafri Rahman Khan

021161011

2. Fariha Rahim Rumi

021161015

Introduction:

We can reduce the settling time by using A PD controller.

We have reduced the settling time of the RLC circuit by 1/2.

$$T_s(\text{new}) = T_s * (1/2)$$


What is controller

- A controller is a device that generates an output signal based on the input signal it receives
- The input signal is actually an error signal ,which is the difference between the measured variable and the desired value

What Is PD Controller?

- A proportional derivative controller (PD controller), as its name indicates, is a controller with a “proportional action” and a “derivative action”.
- The proportional action is an action proportional to the variable controlled or its error (difference between the desired value and the actual value of the controlled variable); this basically means that a gain multiplies either the variable or its error compared to the desired value.
- The derivative action is an action that implies the derivative of the controlled variable. This usually means that the variable is derived, then multiplied by a gain



Given RLC Circuit:

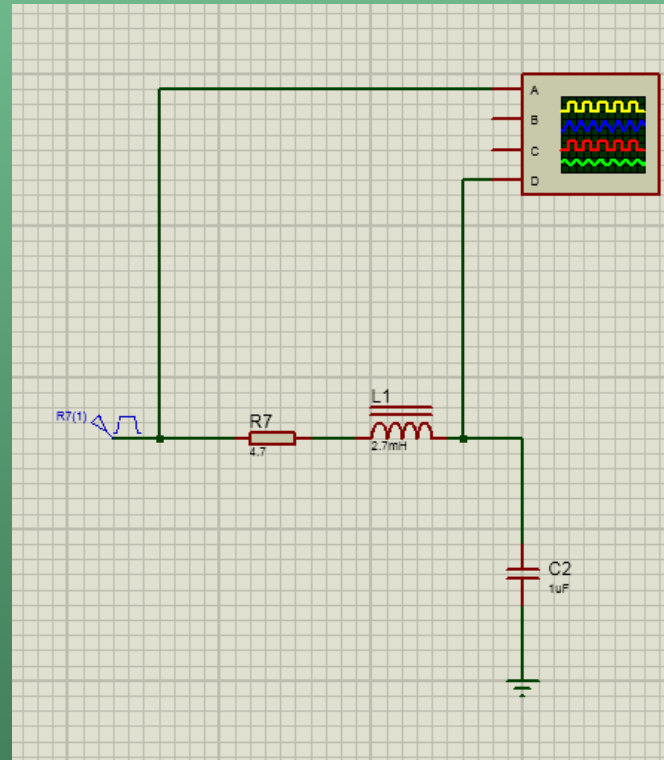



Procedure:

1. Using SISO Design tool, create the design for a unity negative feedback system with $G(s)$ and plot the root locus.
2. Draw the zeta line for required overshoot. Select the closed-loop pole at the intersection of shadowed region and the root locus.
3. Calculate the imaginary part, ω_d and real part, σ_d of the compensated dominant pole from the two-third value of uncompensated peak time and half of uncompensated settling time.
4. Find the Z_c by calculating the pole angle.
5. Put the value of Z_c in pole/zero .

Uncompensated In Proteus :

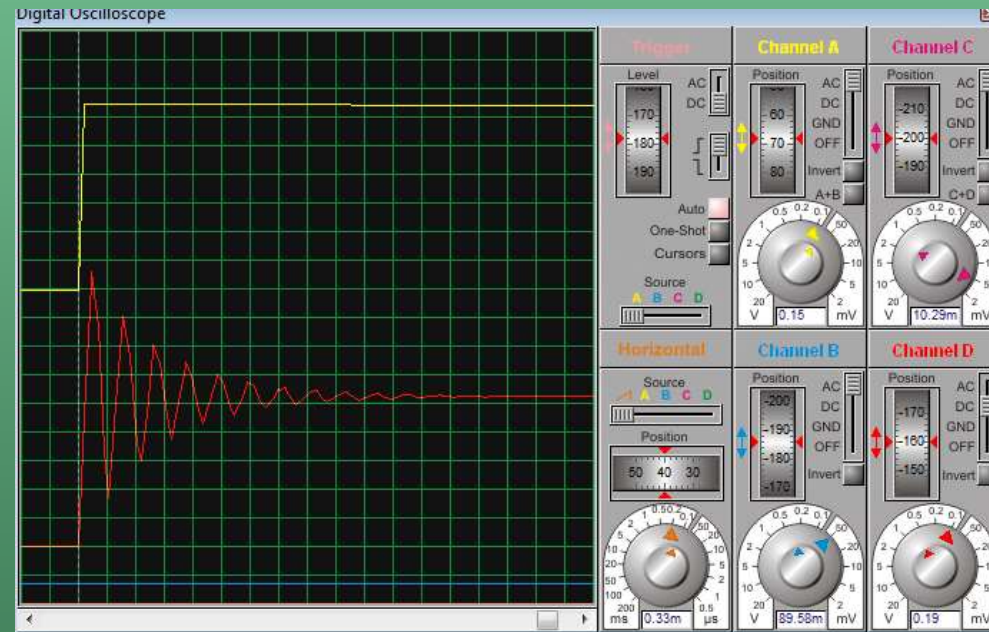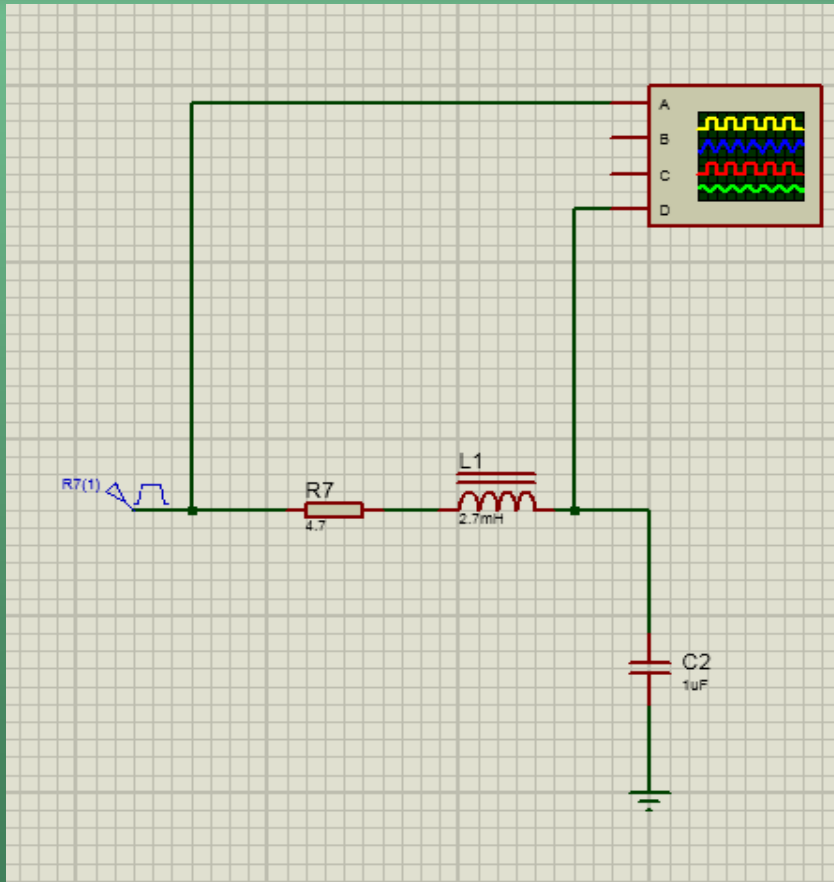

Uncompensated In MATLAB:

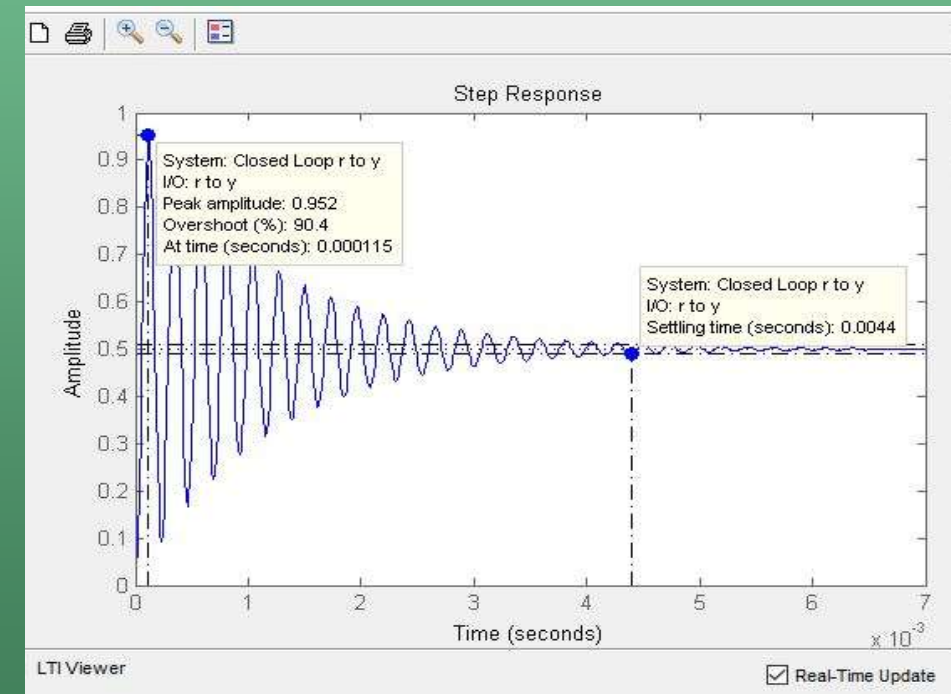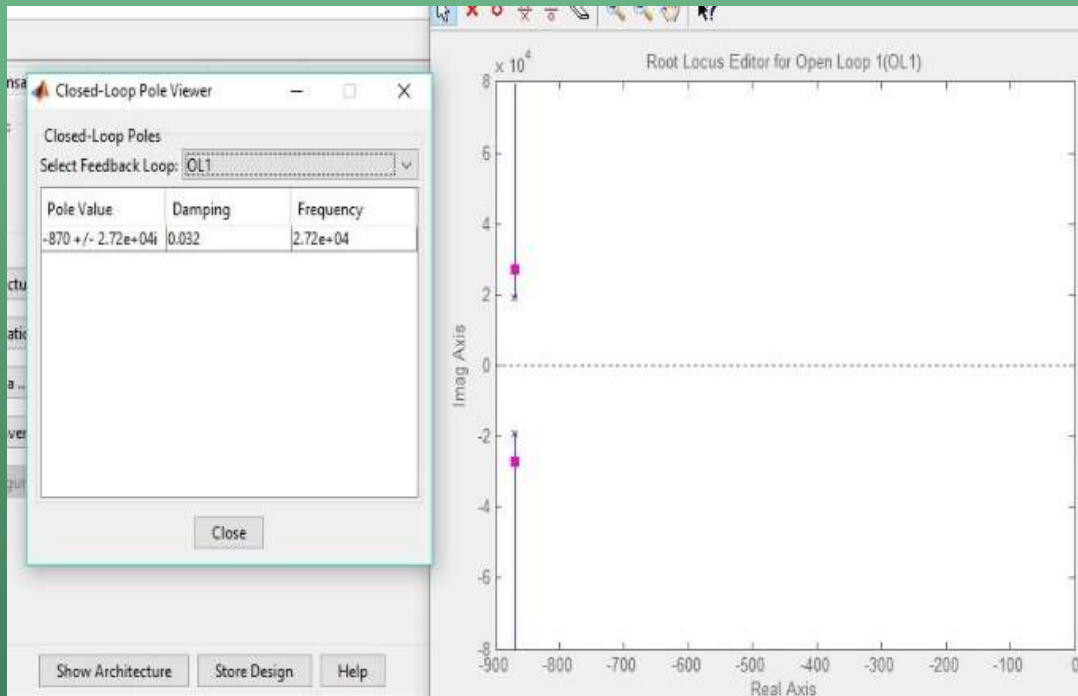

Uncompensated-Compensated(Calculation):

$$G_p = \frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

Same Over Shoot


Maintain Pick Time $\frac{T_p}{2}$

$$\theta_1 = 113.51^\circ$$



$$\theta_2 = 90.83^\circ$$

$$\theta_{zc} = 24.4^\circ$$



$$z_c = 65670.15$$

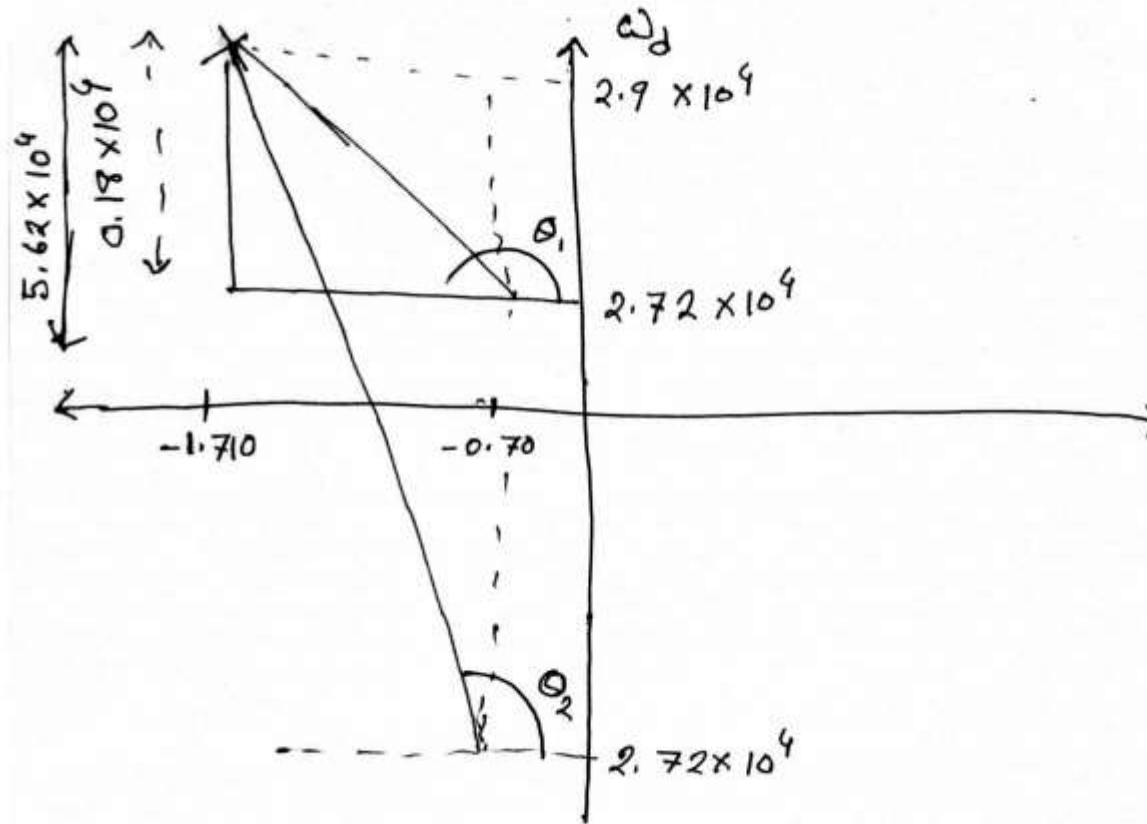

Compensated In MATLAB:

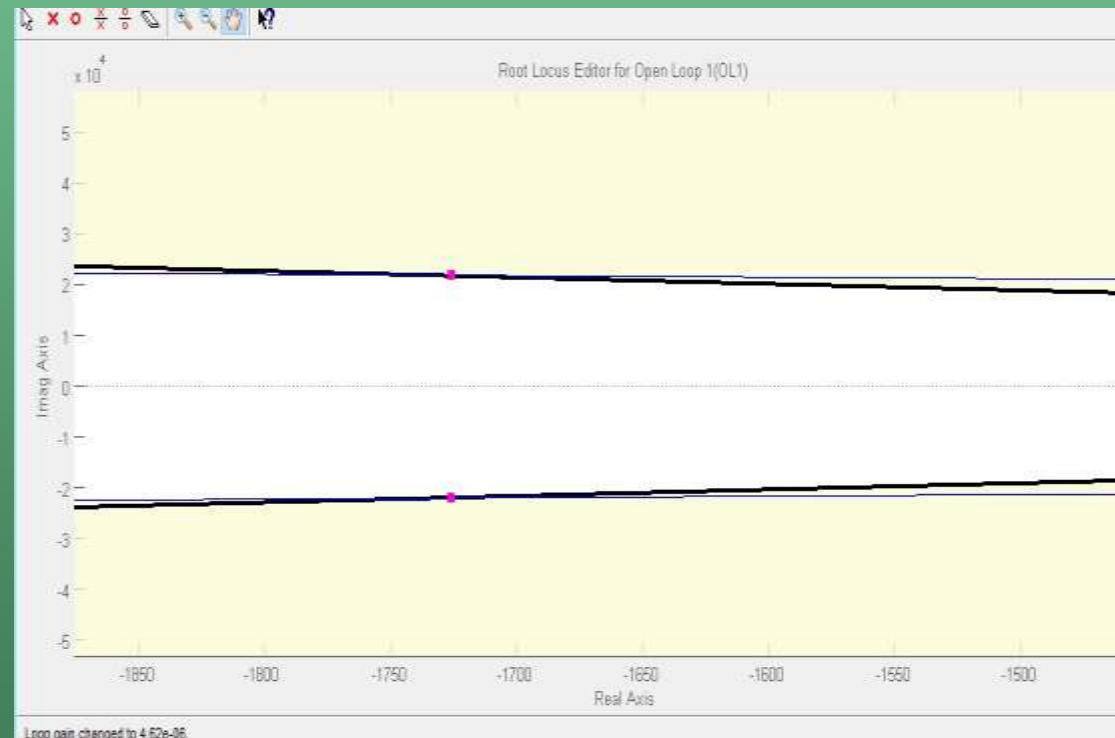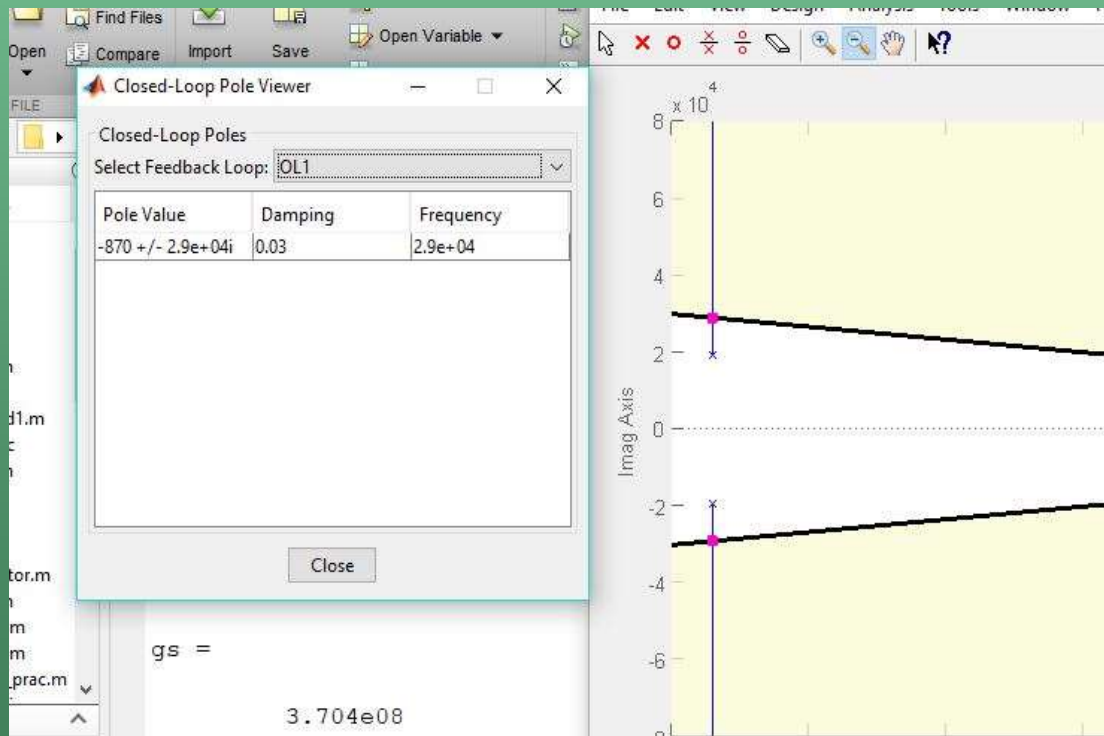

Compensated In Matlab:

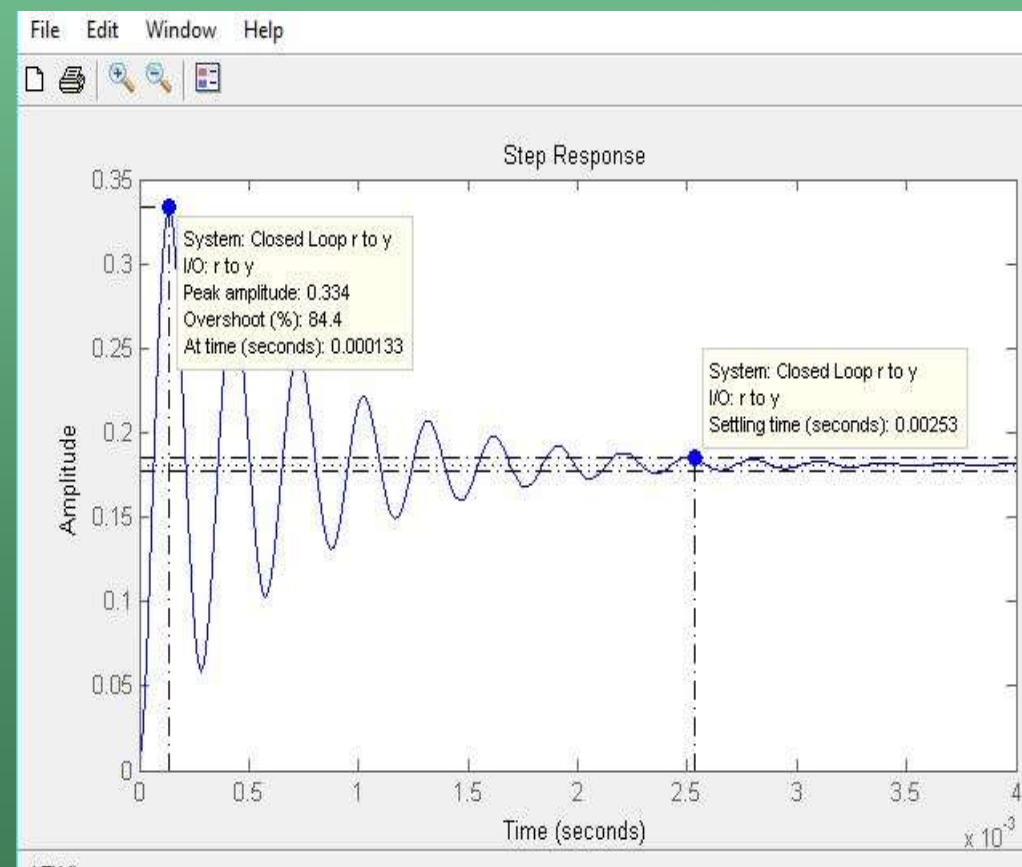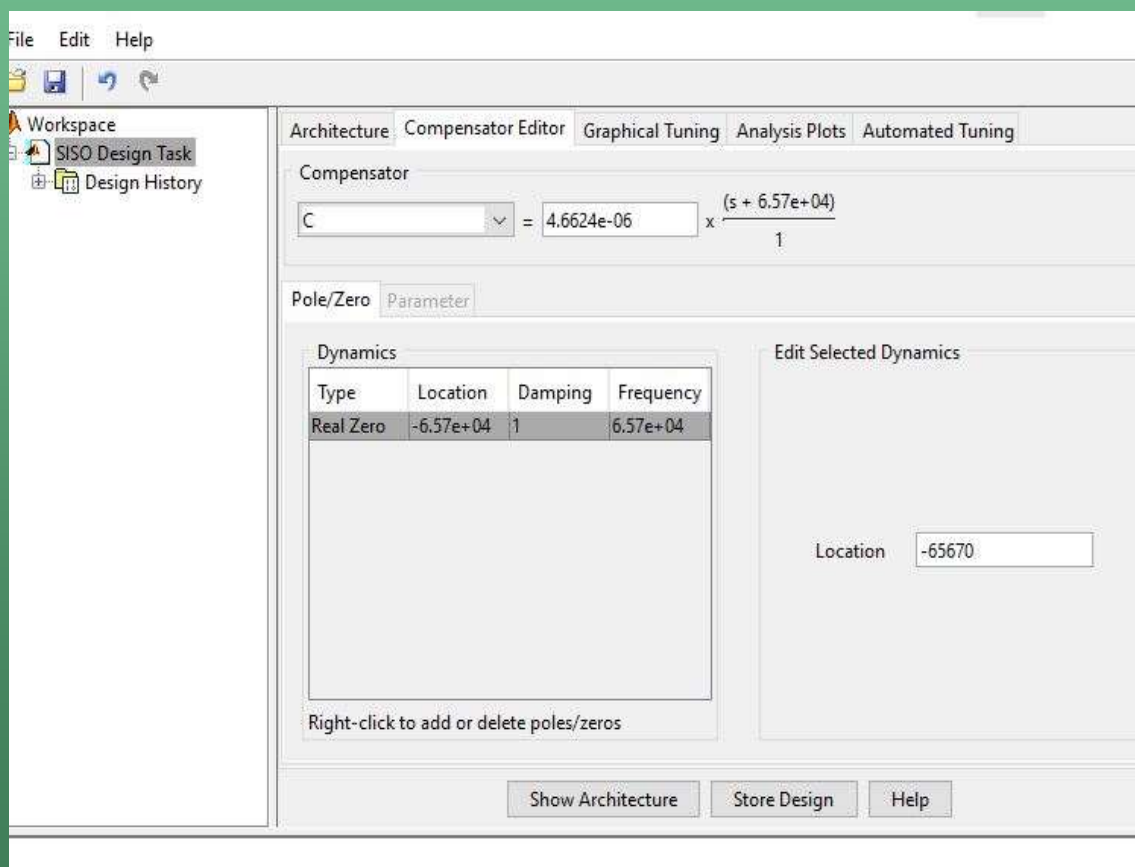

Design pd :

- $PD = K(S + Z_c) = R_2 C(s + 1/R_1 C)$
- $K = 4.66 \times 10^{-6}$ (from matlab)
- $Z_c = 65670.15$ (from hand calculation)

- $1/R_1 \cdot C = Z_c = 65670.15$
6



- $R_1 = 1/(C \cdot Z_c) = 152.2 \text{ ohm}$
ohm

Let, $C = 0.1 \mu\text{F}$

$$R_2 \cdot C = 4.66 \times 10^{-6}$$

$$R_2 = 46.25$$

Implement Circuit In Proteus:

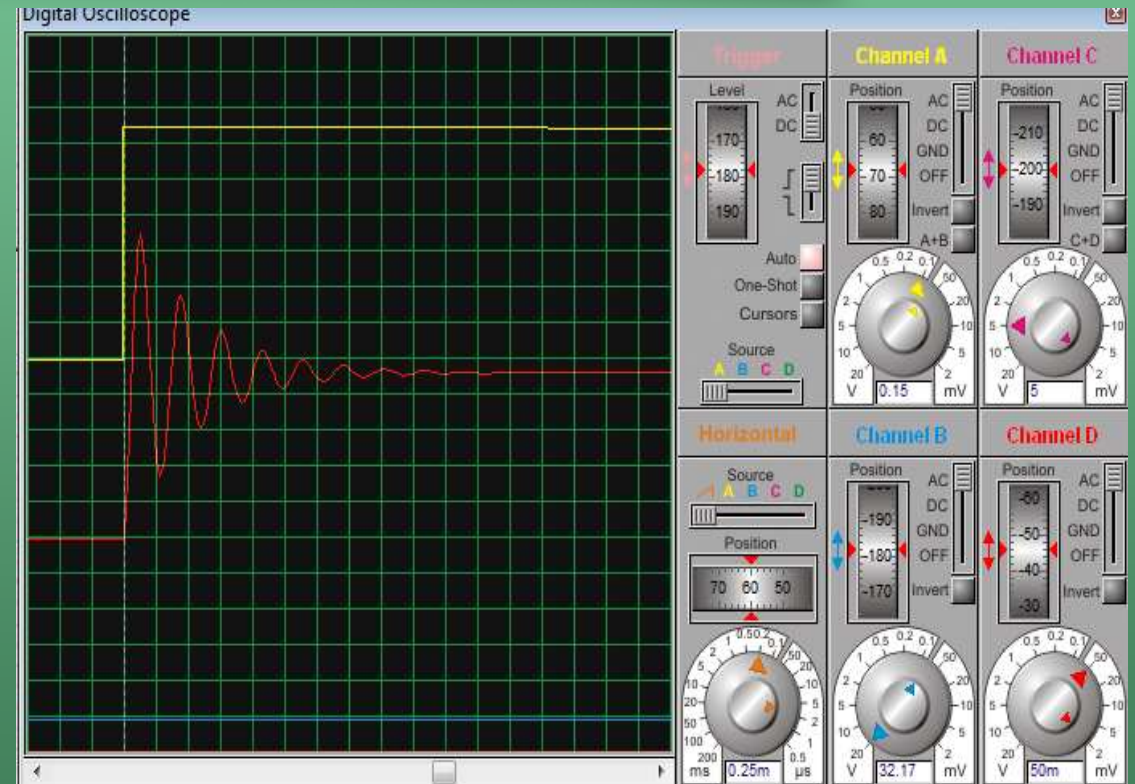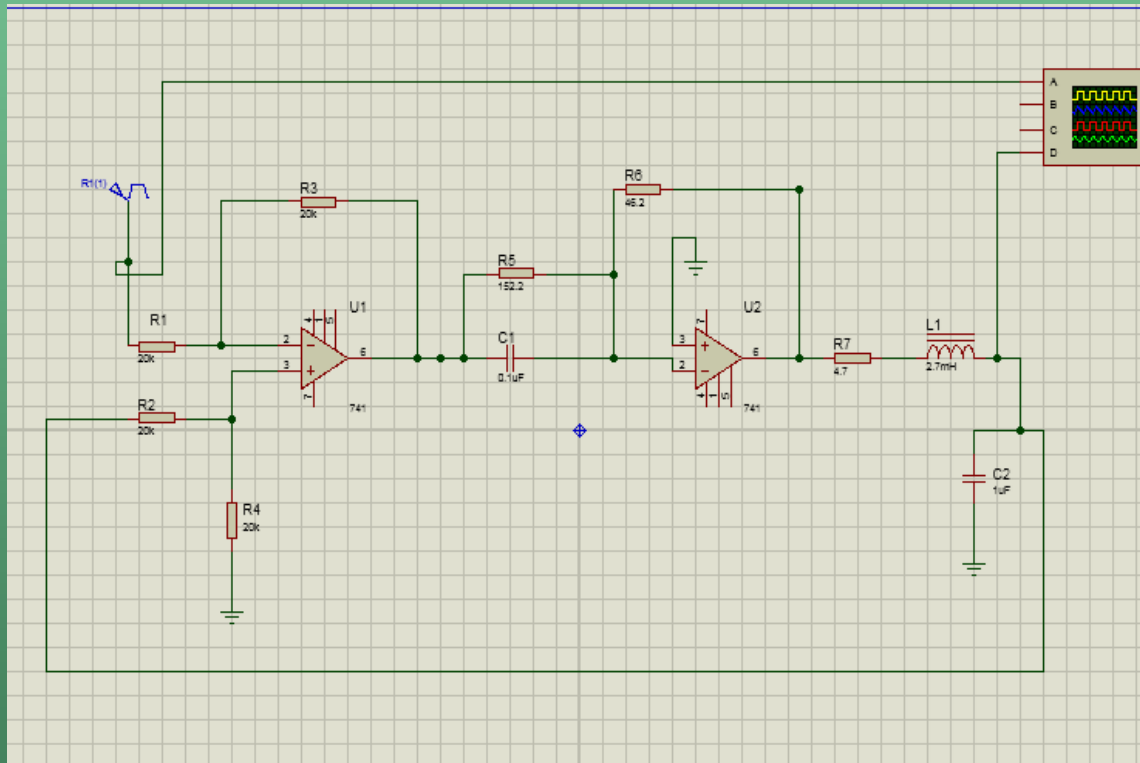

Thank
you!